
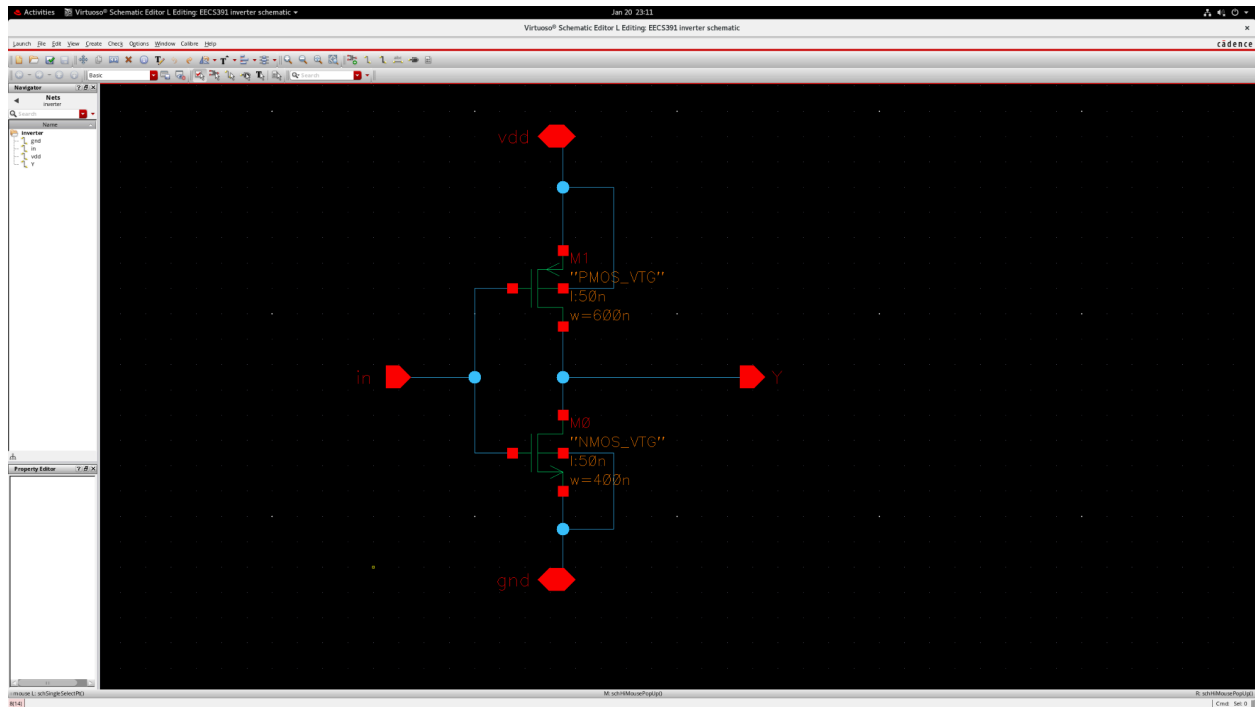


Giovanni Michel
01/24/24
Student iD:3503394

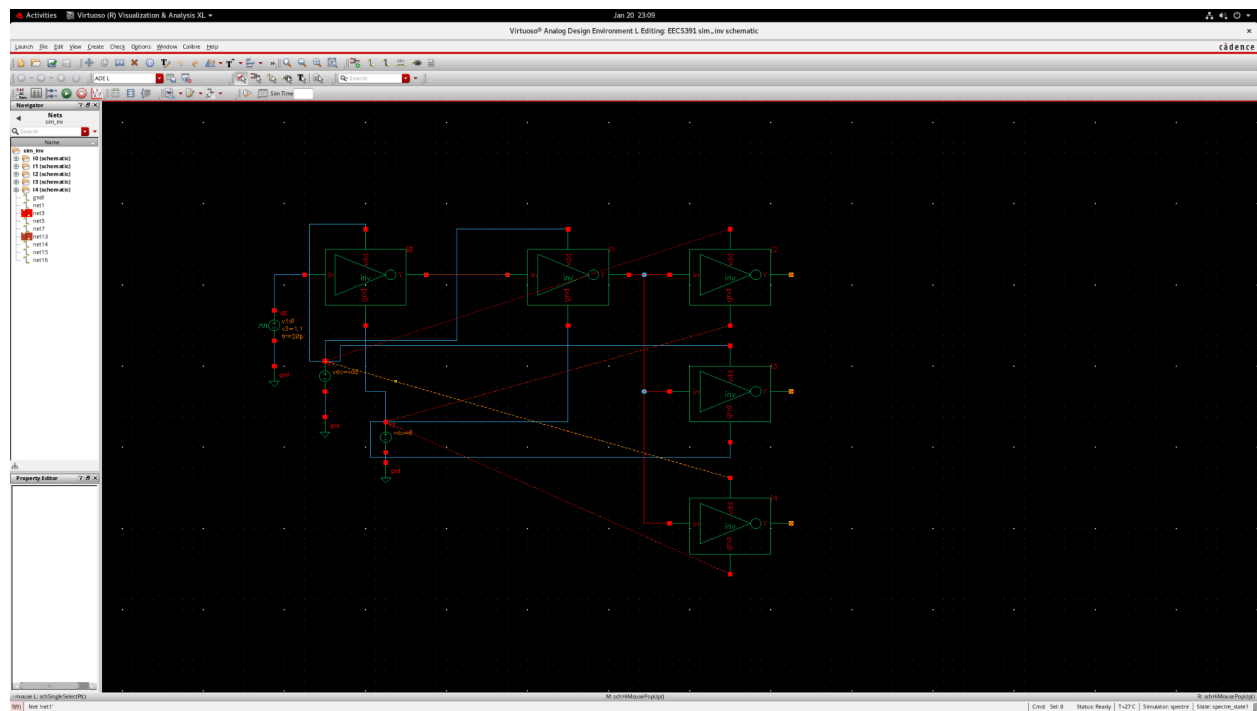
1. Snapshot of your schematics, both inverter and testbench.
 - Here is the snapshot of the schematic I made for the inverter. This is including the connections of the in,out,vdd,and gnd pins.




- Here is the snapshot of the testbench I made to simulate my design.




 2. Snapshot of your layout of single inverter (use ruler shortcut key "k" to show the size of the circuit (from top to bottom, from left to right).





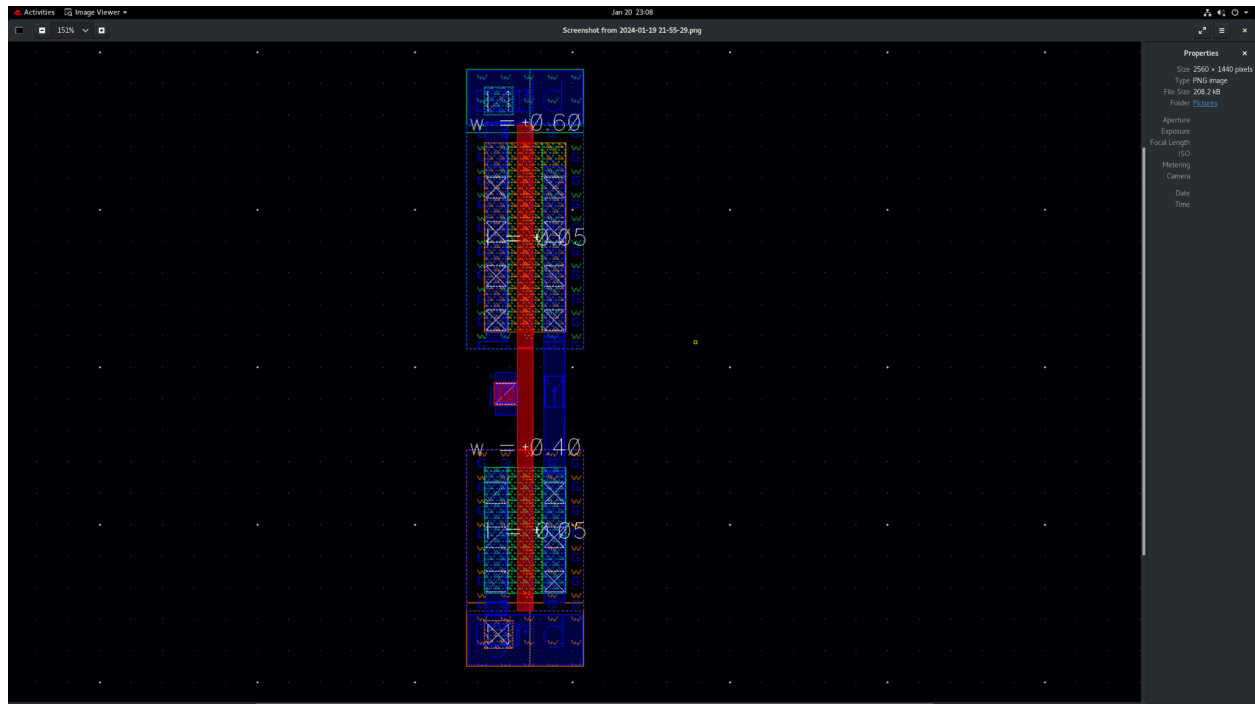

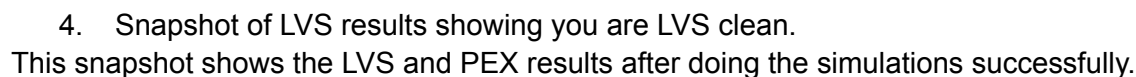3. Snapshot of DRC results showing you are DRC clean.



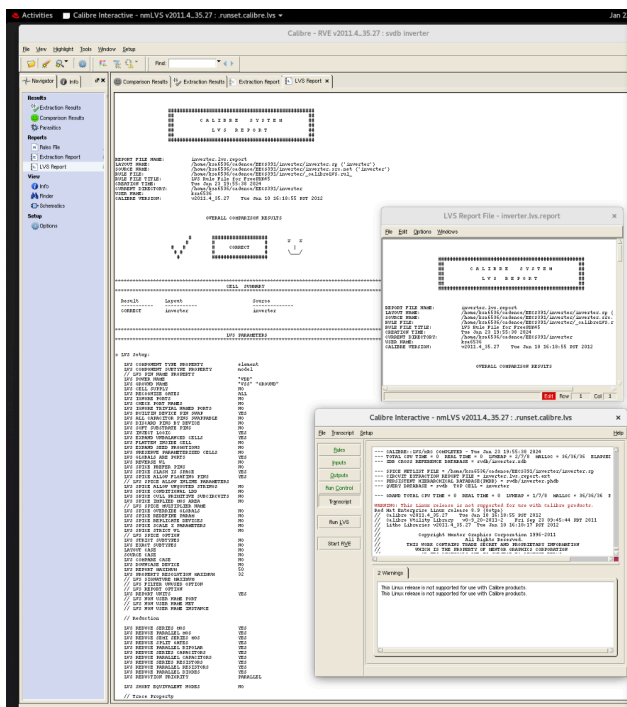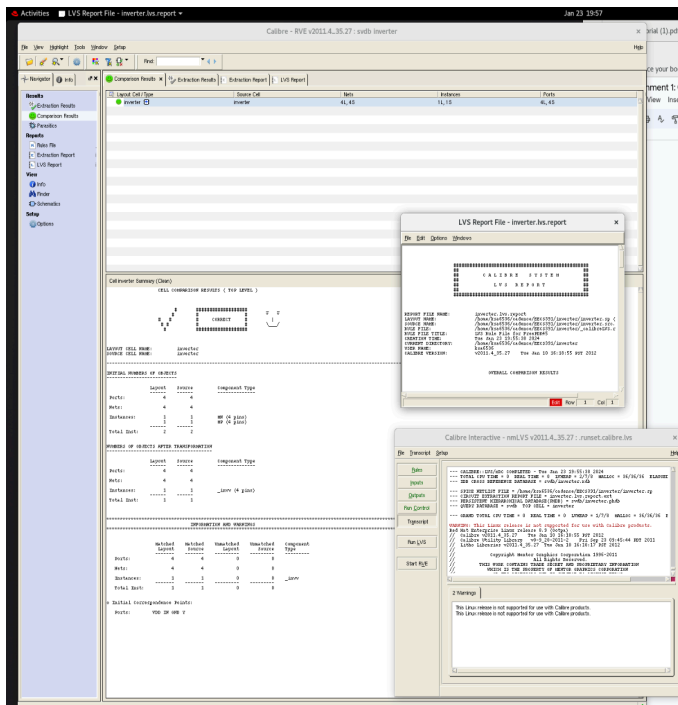
Here I show the layout extraction summary for LVS.




- Both schematic simulation and layout extraction simulation waveforms of the inverter testbench showing input and output transitions. (Use shortcut key "a" and "b" in the waveform window to measure the delay from the input signal to output signal at 50%)

transition points.

Here is the schematic simulation first:

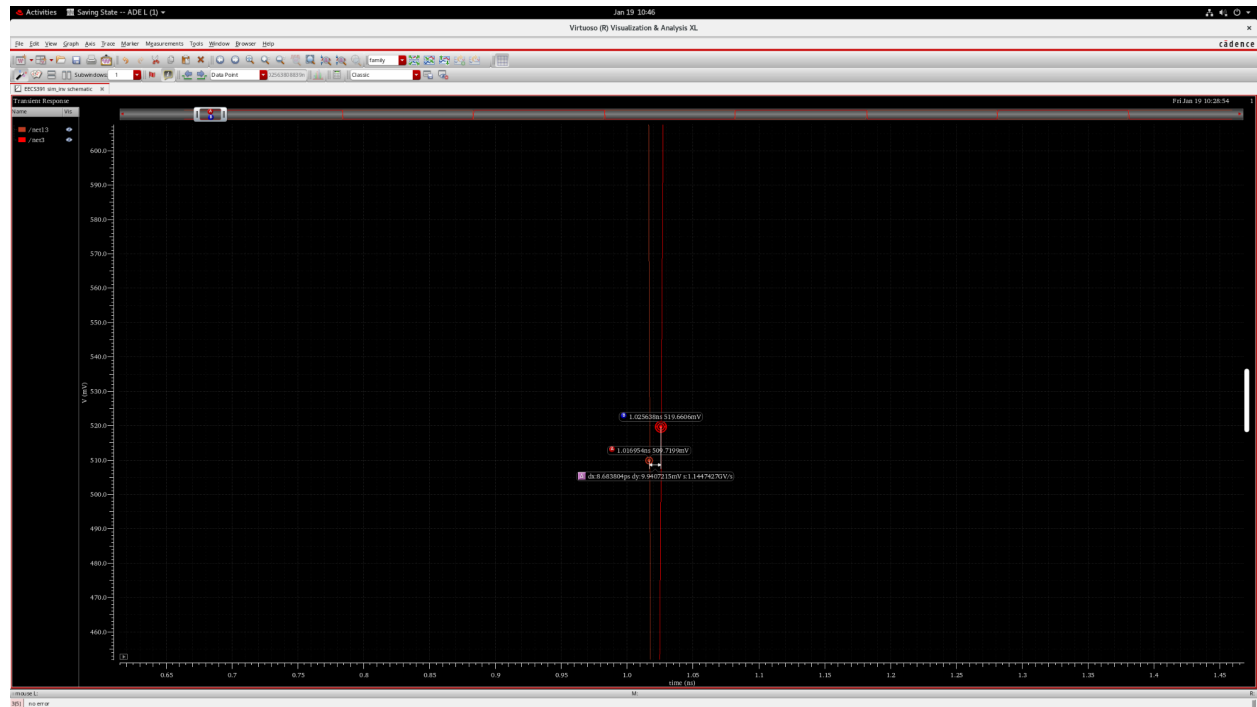

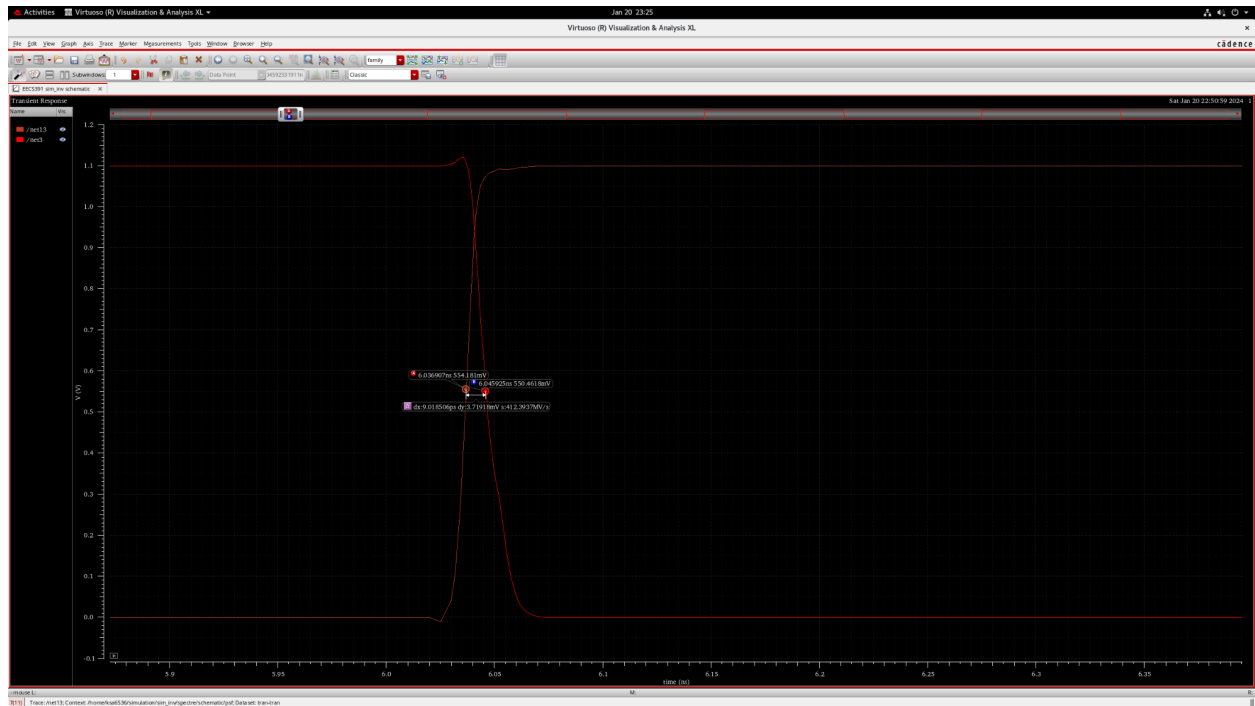Here is the layout extraction simulation:



7. A simulation result table comparing (1) delay time (both rising and falling), (2) transition time (slew rate) from 20% to 80% for both rising and falling, (3) energy during rise and fall transition of the inverter from both schematic and layout extracted simulation.

	Simulated	LVS
Delay Rise	9.065p (Rise)	11.51p
Delay Fall	9.535p (Fall)	11.06p
Energy	7.818f	9.411f
Slew Rate	51.541GV/s	42.643GV/s

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help

cadence JSS

27

Design Variables

Name	Value
vdd	1.1

Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 40n moderate

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1 net13		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2 I1/vdd		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
3 delay_fall	9.065p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
4 energy_rise_fall	7.818f	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5 delay_rise	9.534p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
6 net3		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv

> Results in /home/ksa6536/simulation/sim_inv/spectre/schema

Plot after simulation: Auto Plotting mode: Replace

1(3) Temperature Status: Ready T=27 C Simulator: spectre State: spectre_state1

Value

Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 40n moderate

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1 net13		<input type="checkbox"/>	<input type="checkbox"/>	aliv
2 I1/vdd		<input type="checkbox"/>	<input checked="" type="checkbox"/>	yes
3 delay_fall	11.06p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
4 energy_rise_fall	9.411f	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5 delay_rise	11.51p	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
6 net3		<input type="checkbox"/>	<input type="checkbox"/>	aliv

Plot after simulation: Auto Plotting mode: Replace

